

# Design of active dry electrodes for wireless BCI system

**Presenter : SeungChan Lee**


GIST, Dept. of Information and Communication, INFONET Lab.




Gwangju Institute of  
Science and Technology
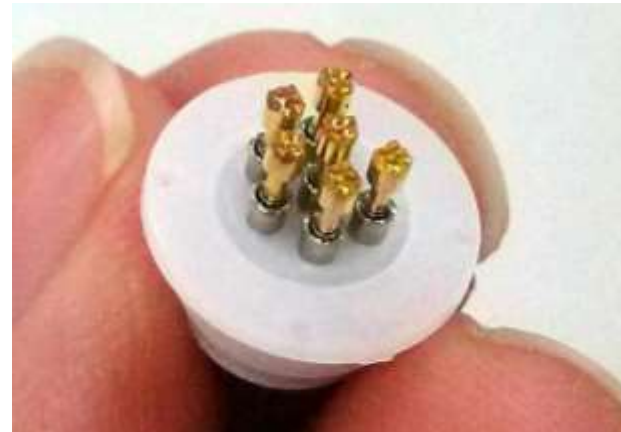
# Introduction

- Development of active dry electrodes
  - For neuro-feedback applications, we are going to design a wireless BCI system.
  - We designed to equip with active dry electrodes for good signal quality and convenient installation.
  - I designed active dry electrodes with impedance converter(OPAMP buffer circuit) and low pass filter.
- Picture of active dry electrodes




# Electrodes test with Emotiv EPOC

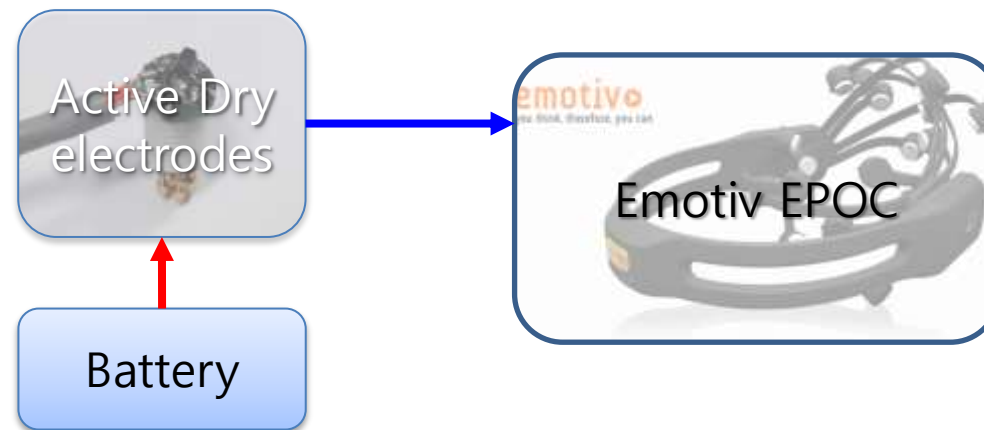

- Test procedure
  - Connect a active dry electrode with Emotiv EPOC headset for measuring signal quality
  - The electrode received power supply from two AA batteries
  - Measure the signal quality using Emotiv test bench utility
- Test results
  - Comparing signal quality with wet electrodes equipped with EPOC headset, the signal quality of designed electrode is unstable and uncorrelated with wet electrodes signals.


# Redesign of electrode circuit

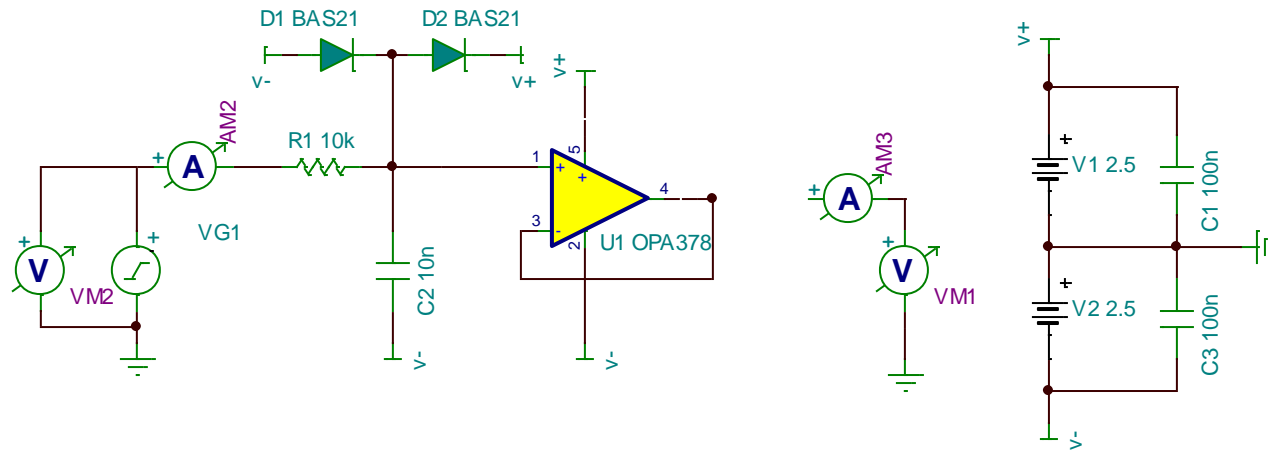


- Previous design of electrode circuit
  - Previous circuit was not working properly with Emotiv EPOC headset due to their unstable signal quality.
- Redesign of electrode circuit
  - RC low pass filter + OPAMP buffer + **Protection circuit**
  - Cutoff frequency of low pass filter = 1591Hz
  - **Bipolar power supply  $\pm 2.5V$**

# Redesign of electrode circuit

- Transient response

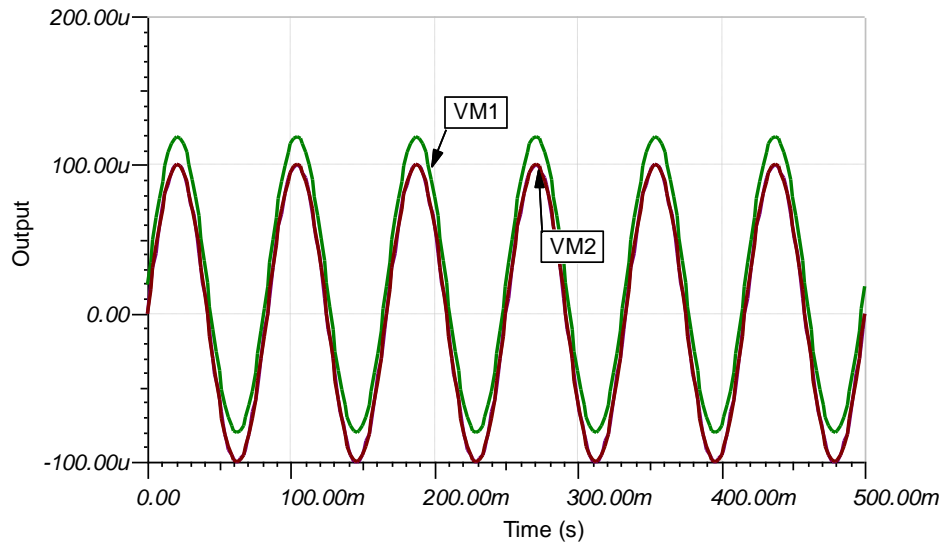

- Frequency response

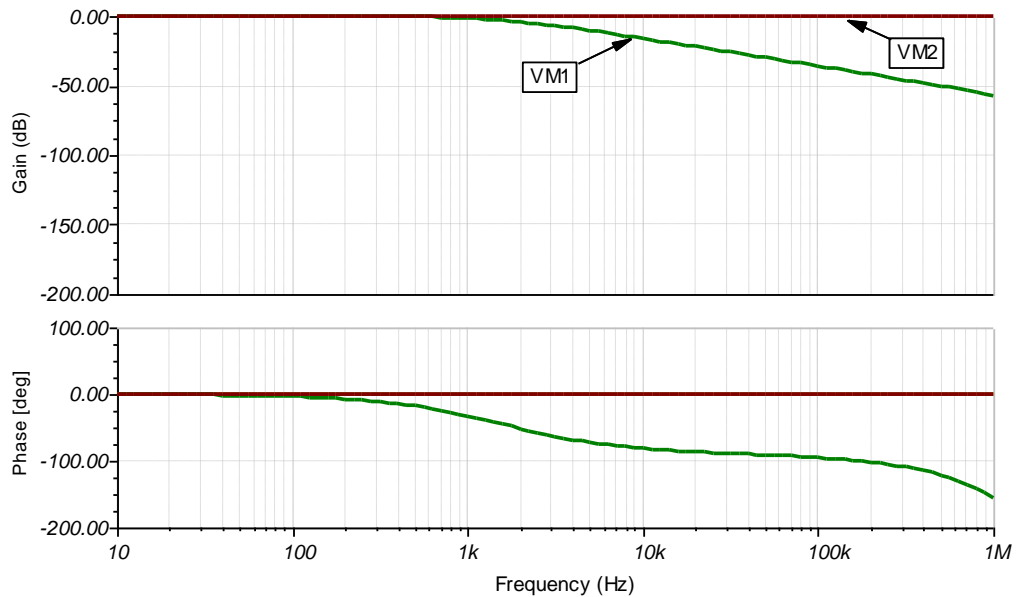

# Electrodes test


- Test method
  - I measured the signal quality and electrodes impedance utilizing ADS1299 evaluation board.
    - The ADS1299 is a complete analog front end IC that including low-noise, multichannel, simultaneous-sampling, 24-bit  $\Delta\Sigma$  ADC with a built-in programmable gain amplifier (PGA), internal reference, and an onboard oscillator for electroencephalogram (EEG) applications.
  - Connecting designed electrodes with evaluation board, I tested our active dry electrodes compared with conventional wet electrodes(Hurev stardisk) on my forehead.


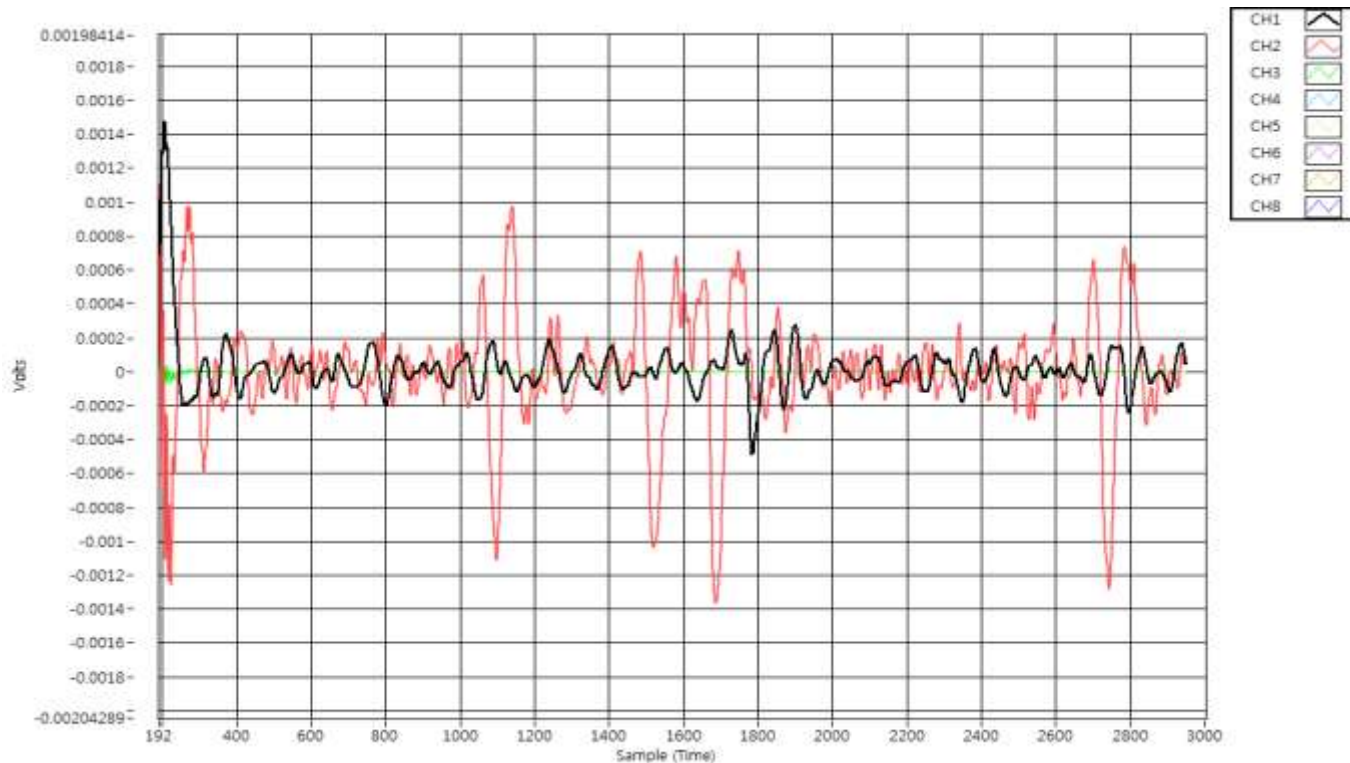
# Electrodes test

- Measured waveforms


- Sampling rate and time : 500 samples/sec, 6 seconds
- Black line : designed active dry electrodes
- Red line : conventional wet electrodes
- Measured EEG signals with designed electrodes looks like less noisy, but phase difference also observed between two measured signals.



# Electrodes test

- Frequency domain of measured waveforms

FFT Magnitude Plot (dB)

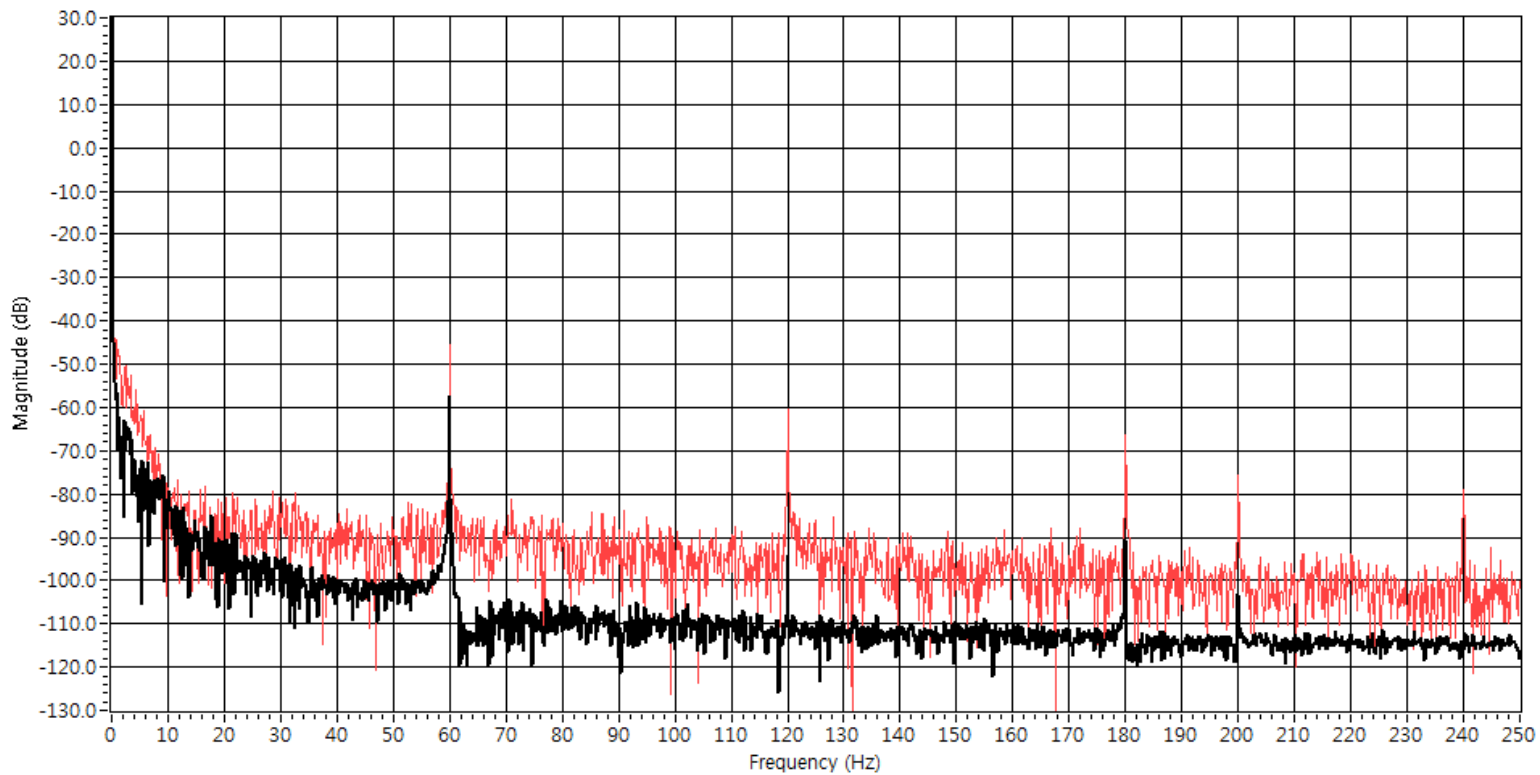



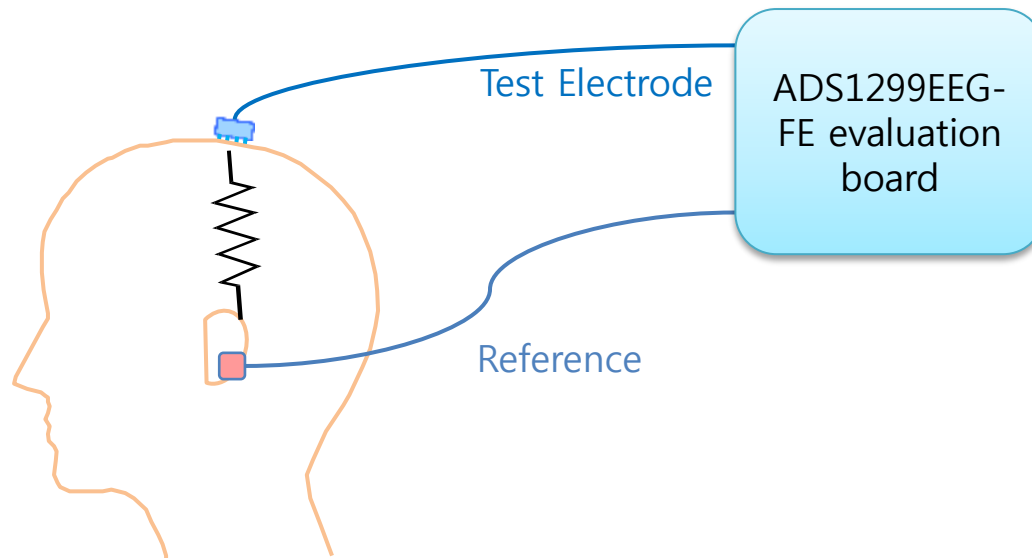
# Electrodes test

- Electrode impedance

- The impedance can be obtained by measuring the voltage difference between a reference electrode and a target electrode.
- Lower impedance means a higher contact capability, and a better contact capability implies high quality EEG signal acquisition.
- ADS1299 has special function for impedance measurement. Using function of AC lead-off detection with 31.25Hz frequency and 6uA current source, I measured electrodes impedance.



# Electrodes test

- Impedance test method

- Measuring peak-to-peak voltage, we can calculate electrodes impedance through Ohm's law.

- Measured peak-to peak voltage

Ch1 : designed electrodes




Ch2 : wet electrodes

	Channel 1	Channel 2
Mean (V)	-226.81E-3	-52.08E-3
Vrms	3.423019E+0	55.194730E-
Vpp	8.09E+0	64.86E-3

- Impedance calculations


- Designed electrodes =  $8.09V/6\mu A = 1.348M\Omega$

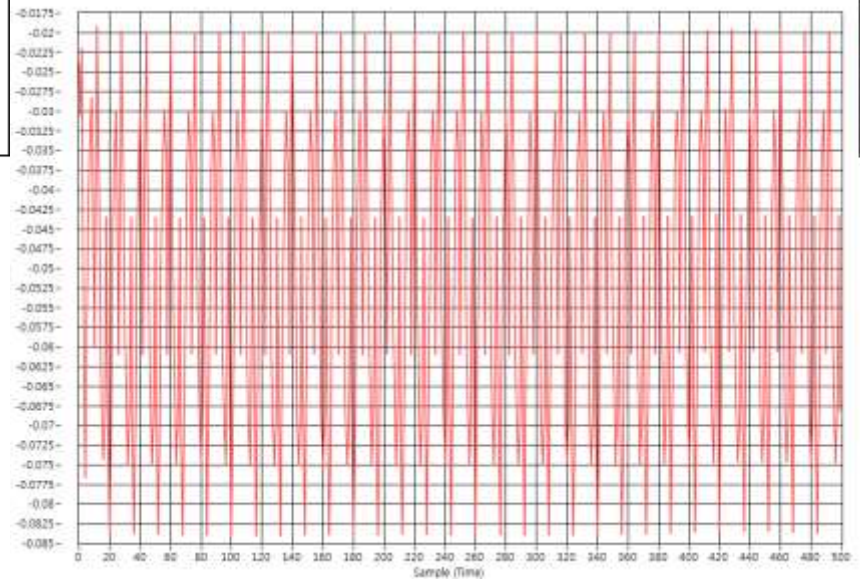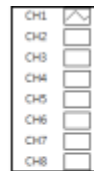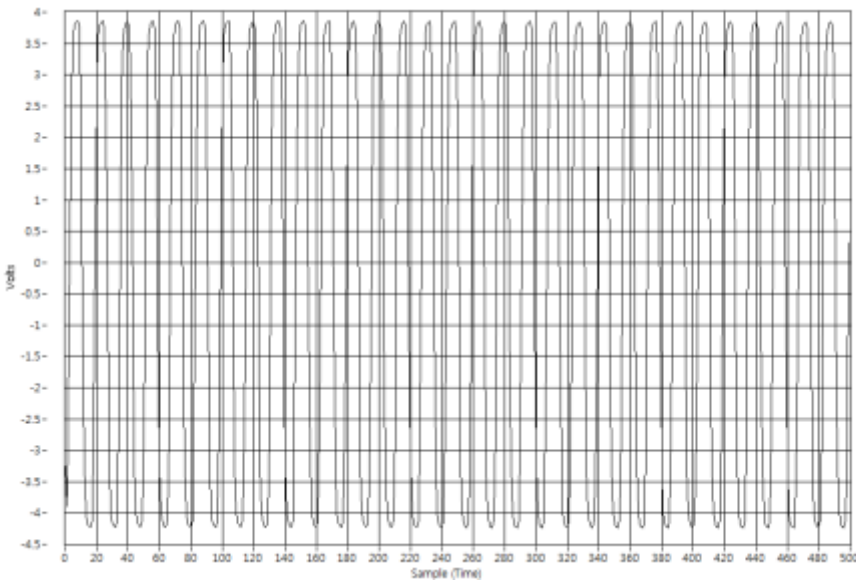- Wet electrodes =  $64.86mV/6\mu A = 10.81k\Omega$



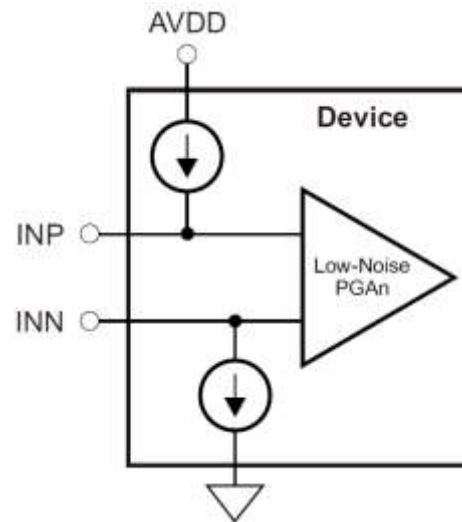
# Electrodes test

- Discussion about designed electrode impedance
  - The impedance of designed electrodes reached  $1.348\text{M}\Omega$ .
  - This is because operational amplifier buffer on designed electrodes circuit.
  - Because OPAMP buffer blocks  $6\mu\text{A}$  current flow from ADS1299, the measured voltages reached saturated voltage range.
  - So, for impedance measurement, we have to find another way.



# G.tec active electrodes circuit

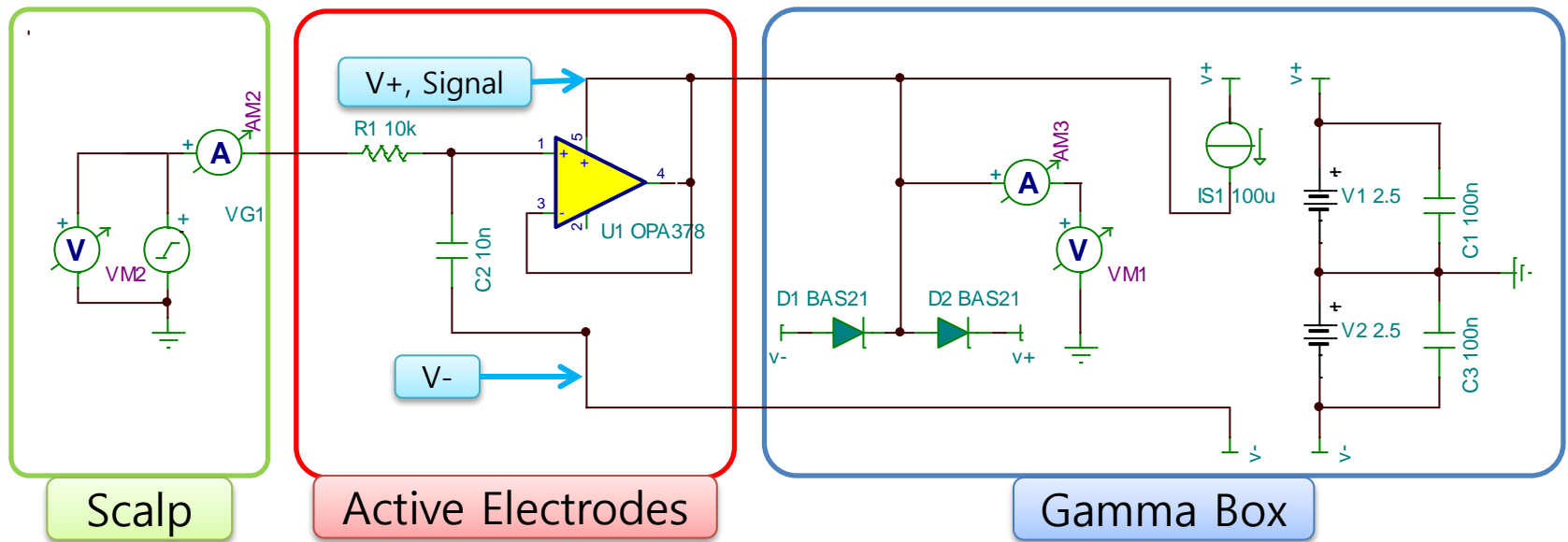


- Structure of g.tec active electrodes


- Used only two wire for connection with Gamma box
  - 100uA current source for power supply instead of voltage source
  - Sharing power supply line and measured signal transmission line
- RC low pass filter + OPAMP buffer

# G.tec active electrodes circuit

- Transient response

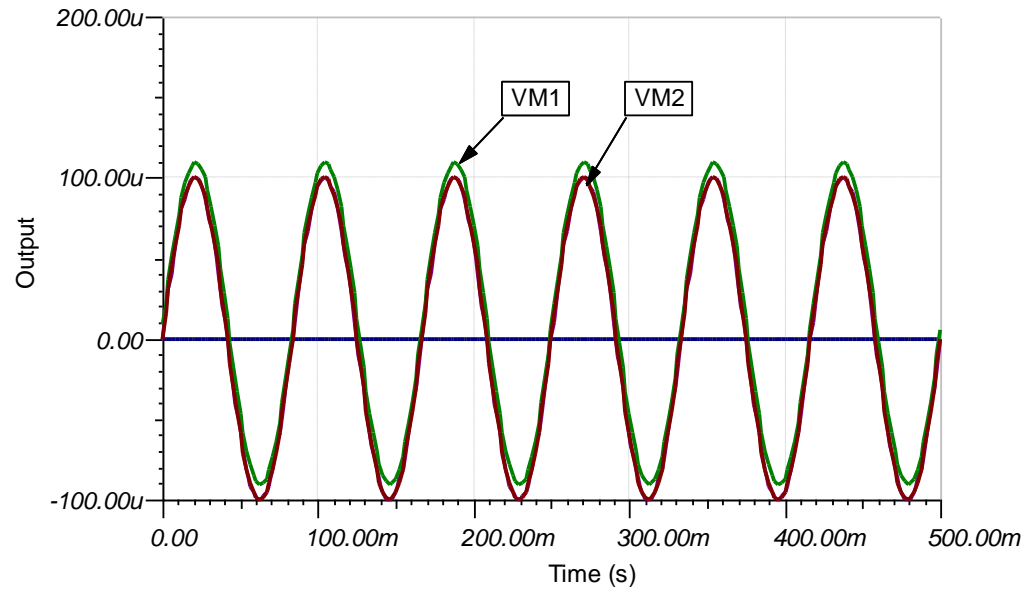

- Frequency response

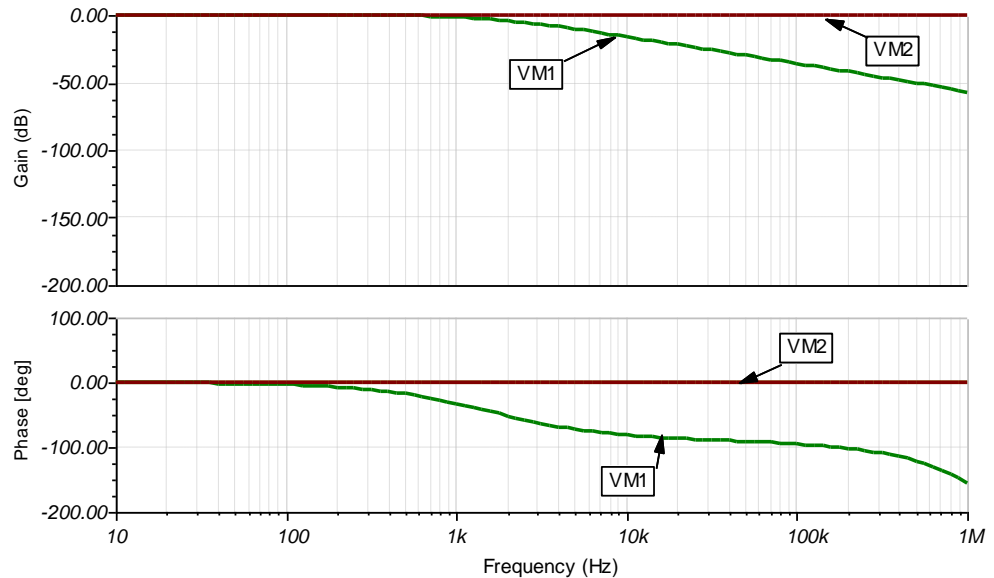

# Wireless BCI system design

- Future work
  - Design of wireless BCI system based on ADS1299 and MSP430 microcontroller.
  - Measurement of impedance about active dry electrodes.
  - Test of g.tec active electrode circuit.

